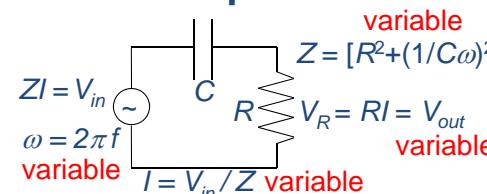


Circuits Filtres

© 2015 Quim Trullàs

Aquestes transparències es poden utilitzar amb fins educatius no comercials, sempre que s'indiqui l'autoria
These transparencies may be used for educational non-commercial purposes so long as the source is attributed

Circuit RC passa-alts




$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{RI}{ZI} = \frac{R}{\sqrt{R^2 + (1/C\omega)^2}}$$


$$H(\omega = \omega_0 = 1/RC) = \frac{1}{\sqrt{2}}$$

$\omega_0 \equiv$ pulsació de tall
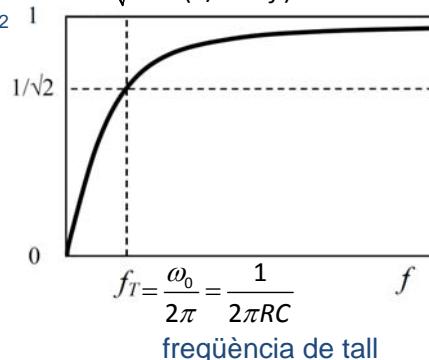
$$H(f) = \frac{R}{\sqrt{R^2 + (1/C2\pi f)^2}}$$



Circuit RL passa-baixos

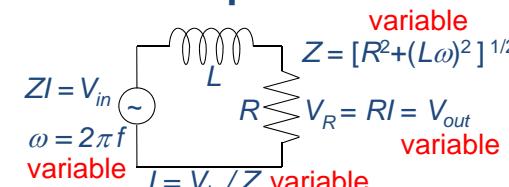


$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{RI}{ZI} = \frac{R}{\sqrt{R^2 + (L\omega)^2}}$$


$$H(\omega = \omega_0 = R/L) = \frac{1}{\sqrt{2}}$$

$\omega_0 \equiv$ pulsació de tall
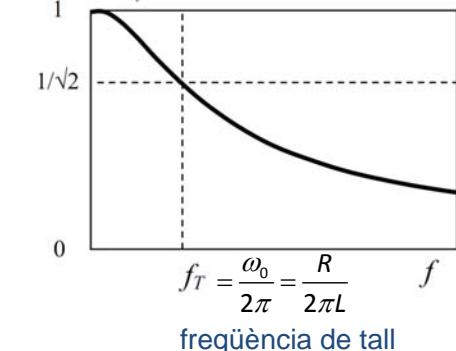
$$H(f) = \frac{R}{\sqrt{R^2 + (L2\pi f)^2}}$$



Circuit RLC passa-banda

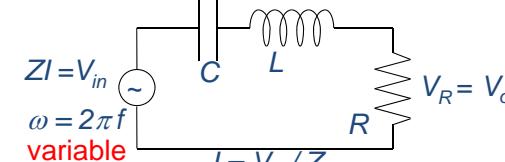

$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{RI}{ZI} = \frac{R}{\sqrt{R^2 + (L\omega - 1/C\omega)^2}}$$

$$H(\omega = \omega_0 = 1/\sqrt{LC}) = 1$$

freqüències de tall passa-baixos i passa-alts

$$f_L = \frac{1}{2\pi} \left[\sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \mp \frac{R}{2L} \right] = \sqrt{(\frac{1}{2}\Delta f)^2 + f_R^2} \mp \frac{1}{2}\Delta f$$

ampla de banda $\Delta f = R/(2\pi L) = f_H - f_L$

factor de qualitat $Q = f_R / \Delta f = (L/C)^{1/2} / R$

$$H(f) = \frac{R}{\sqrt{R^2 + (L2\pi f - 1/C2\pi f)^2}}$$

